

Department of Electrical and Computer Engineering
Queen's University
ELEC 374 Digital Systems Engineering
Laboratory Project

Winter 2024

Designing a Simple RISC Computer (Mini SRC): Phase 2

1. Objectives

The objective of this project is to design, simulate, implement, and verify a simple RISC Computer (Mini SRC), consisting of a simple RISC processor, memory, and I/O. Phase 2 of this project consists of the design and Functional Simulation of the rest of the Mini SRC datapath. This includes the circuits associated with the “Select and Encode” logic, “Memory Subsystem”, “CON FF” logic, and “Input/Output” ports, as well as load/store instructions, branch and jump instructions, and immediate instructions. You will add the necessary logic circuits to the Datapath circuitry built in Phase 1.

You are to simulate the Load and Store instructions *ld*, *ldi*, and *st*, to test the “Memory Subsystem” and the “Select and Encode” logic. Your simulations will also include the *addi*, *andi*, and *ori* ALU instructions, the conditional Branch Instructions *brzr*, *brnz*, *brmi*, and *brpl* in order to test the “CON FF” logic, the *jr* and *jal* instructions, the *mfhi* and *mflo* instructions, as well as the *in* and *out* instructions to test the “Input/Output” ports. Design input can be done using an all HDL approach. Testing will be done by Functional Simulation.

2. Preliminaries

2.1 The Memory Subsystem

As shown in Figure 1, the “Memory Subsystem” includes the Memory Address Register (MAR), the Memory Data Register (MDR), and the RAM Memory Component.

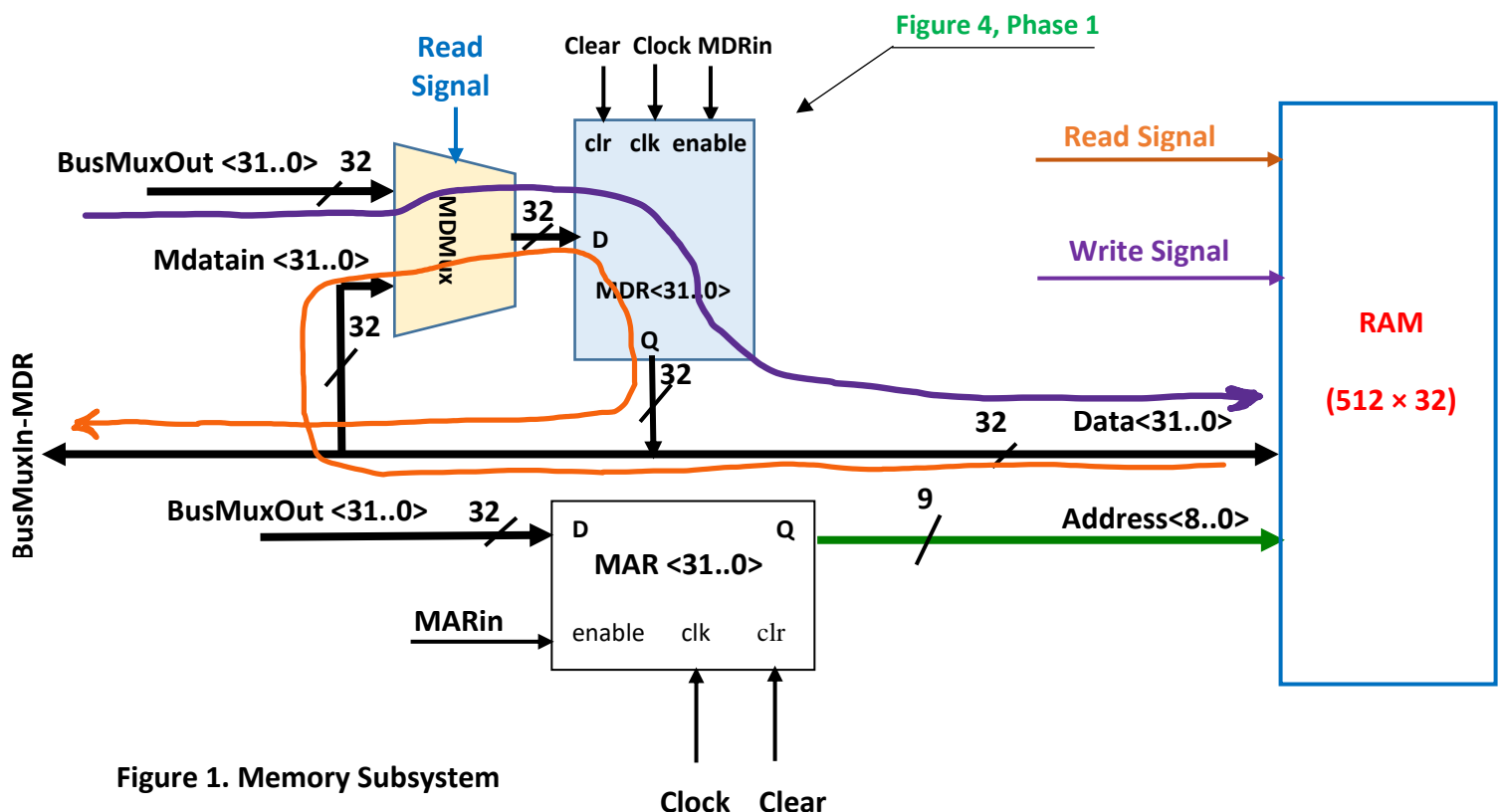


Figure 1. Memory Subsystem

You may write your own Verilog or VHDL code for the (synchronous or asynchronous) RAM, or you may choose a RAM component from the Library. The Read and Write control signals are the signals to the memory for Read and Write operations and may need to be latched if the memory is slow. These signals are generated by the Control Unit in Phase 3. A synchronous memory would work fine for this project. However, if the memory is asynchronous, then you may need to generate a Completion signal from the memory interface to let the Control Unit know when data becomes available.

2.2 The Select and Encode Logic

Figure 2 shows the block diagram for the “Select and Encode” logic. In Phase 1, in order to test the datapath, we used the $R0in - R15in$ and $R0out - R15out$ signals as external inputs. In this phase, we generate these signals internally by the “Select and Encode” logic.

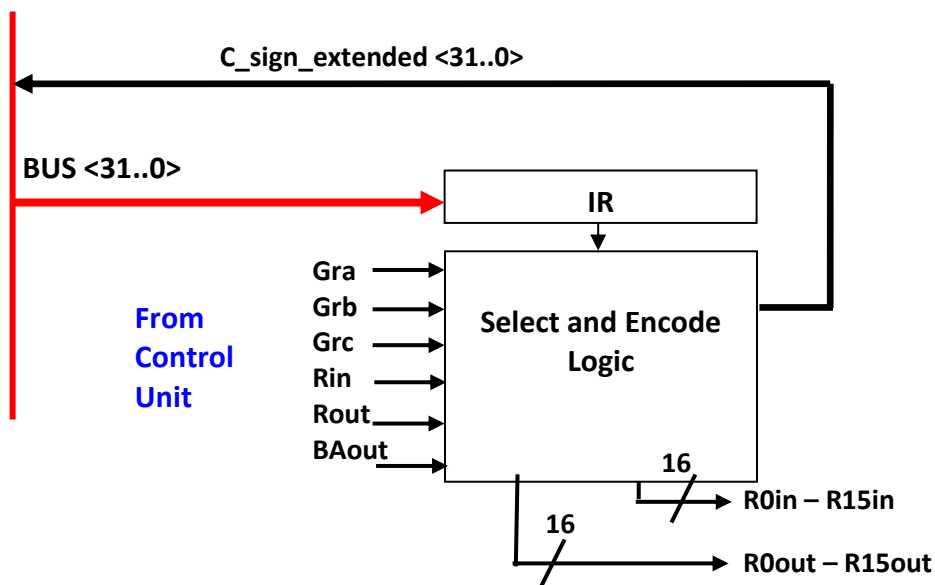


Figure 2. Select and Encode block diagram

As shown in Figure 2 and Figure 3, the “Select and Encode” logic accepts the Gra , Grb , Grc , Rin , $Rout$, and $BAout$ signals as external inputs. In Phase 3, these signals will be generated internally by the Control Unit. The new control signals $R0in - R15in$ and $R0out - R15out$ signals are derived by selecting the appropriate 4-bit fields for Ra , Rb , and Rc in the IR register, using the Gra , Grb , or Grc control signal, and decoding them along with the Rin , $Rout$, and $BAout$ control signals (consult the Instruction Formats in the [CPU Specification](#) document). The logic needed for the case of only 16 registers in Mini SRC is shown in Figure 3. The general version of this design for the SRC that has 32 general-purpose registers is shown in Figure 4.4 on page 148 of the Lab Reader.

The $BAout$ (base address) signal, when asserted, gates 0's onto the bus if $R0$ is selected (see the revisions to $R0$ circuitry in Figure 5 of this document) in the Load and Store instructions; otherwise, it will put the contents of one of the selected registers $R1 - R15$ onto the bus.

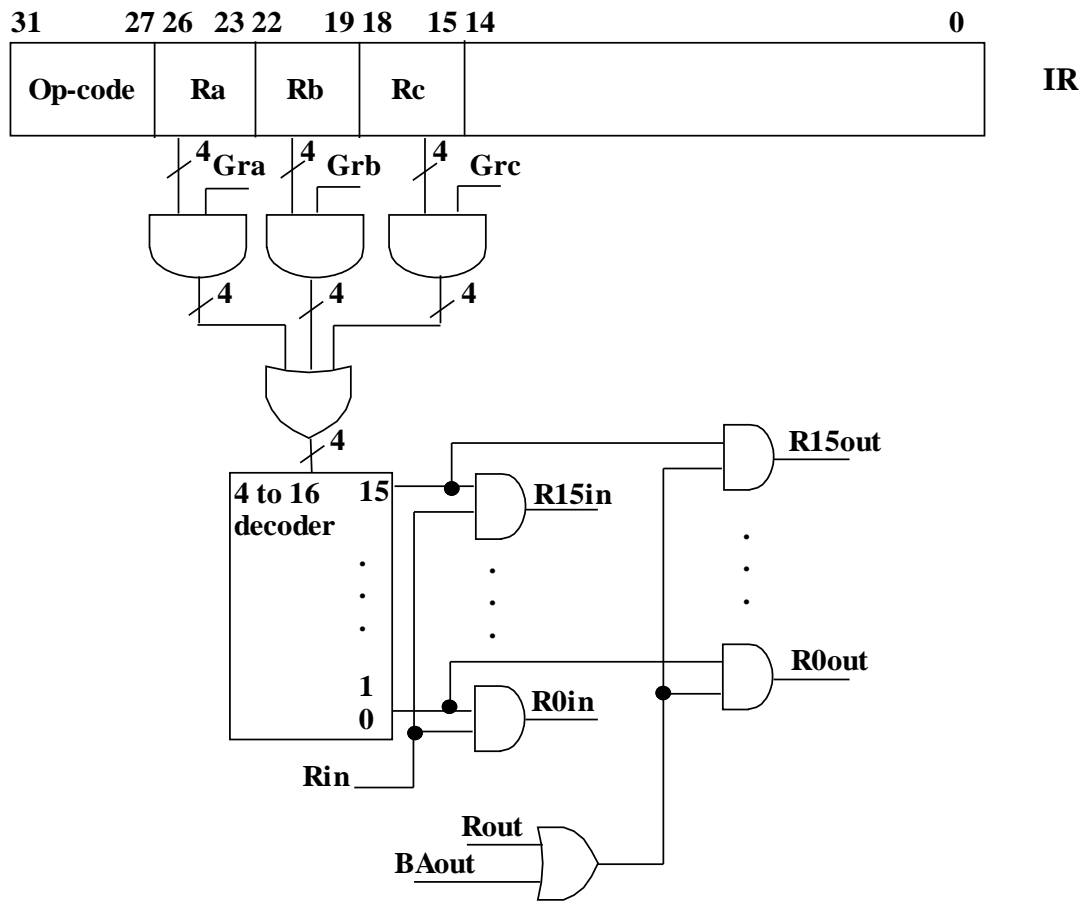


Figure 3. "Select and Encode" logic to generate R0in-R15in and R0out-R15out

To support 2's complement numbers in Load/Store (*ld*, *ldi*, and *st*) instructions as well as ALU immediate (*addi*, *andi*, and *ori*) instructions, the constant C in the IR needs to be sign-extended to 32 bits. The logic needed in Mini SRC is shown in Figure 4 (similar to Figure 4.5 on page 150 of the Lab Reader). The sign-extension is done by fanning out the msb of the appropriate field (IR<18>) to all the higher-order bits.

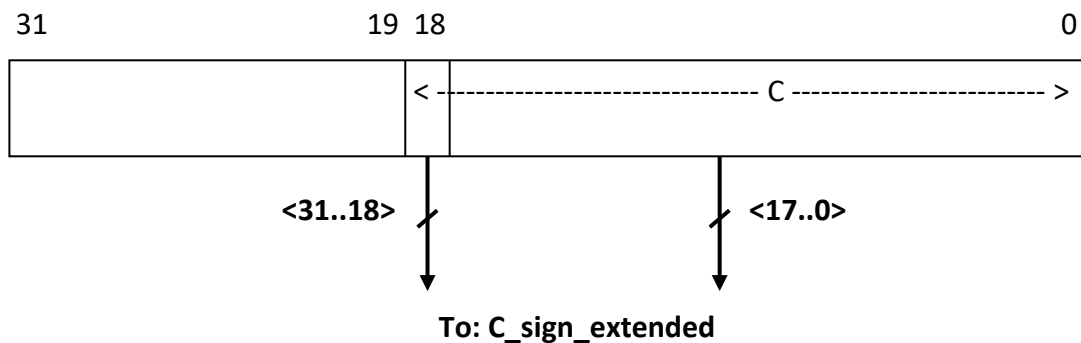


Figure 4. Sign extension of constant C

2.3 Revision to Register R0

The specification of the Load and Store instructions (*ld*, *ldi*, *st*) in Mini SRC (see the [CPU Specification](#) document) suggests that depending on the chosen register R_b, the effective address/data is either the constant C (when R_b = R0), or the constant C plus the contents of the specified R_b register (when R_b ≠ R0). As discussed earlier, the *BAout* signal gates 0's onto the bus if R0 is selected, or it gates the selected register's contents if one of the registers R1 – R15 is selected. To support the Load and Store instructions, the register R0 circuitry will then need to be revised as shown in Figure 5.

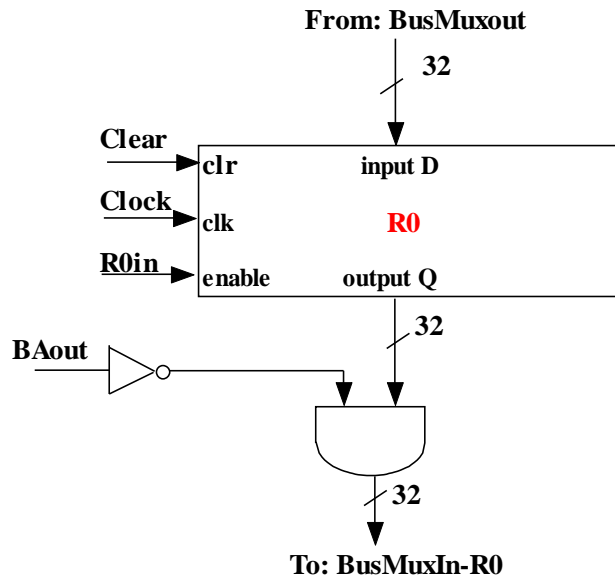


Figure 5. Revised register R0

2.4 The “CON FF” Logic

Figure 6 shows the block diagram for the “CON FF” logic. The “CON FF” logic is used to determine whether the correct condition has been met to cause branching to take place in a Conditional Branch instruction.

 


Figure 6. CON FF logic

- Conditional Branch Instructions
brzr, brnz, brmi, brpl

As described in the Mini SRC specification, the branch instruction has the following format:



Branch $PC \leftarrow PC + 1 + C$ (sign-extended) if $R[Ra]$ meets the condition

C2 field:	--00: branch if zero	brzr	Ra, C
	--01: branch if nonzero	brnz	Ra, C
	--10: branch if positive	brpl	Ra, C
	--11: branch if negative	brmi	Ra, C

The signals needed to control branching instructions are derived from the numerical value in register Ra, and from the branching condition in the C2 field, in IR[22..19]. For SRC, the required logic is shown in Figure 4.10 on page 158 of the Lab Reader. We simplify this in Mini SRC, as shown in Figure 7. Note that the CONin signal (connected to the enable input of the CON FF) will be generated by the Control Unit in Phase 3.

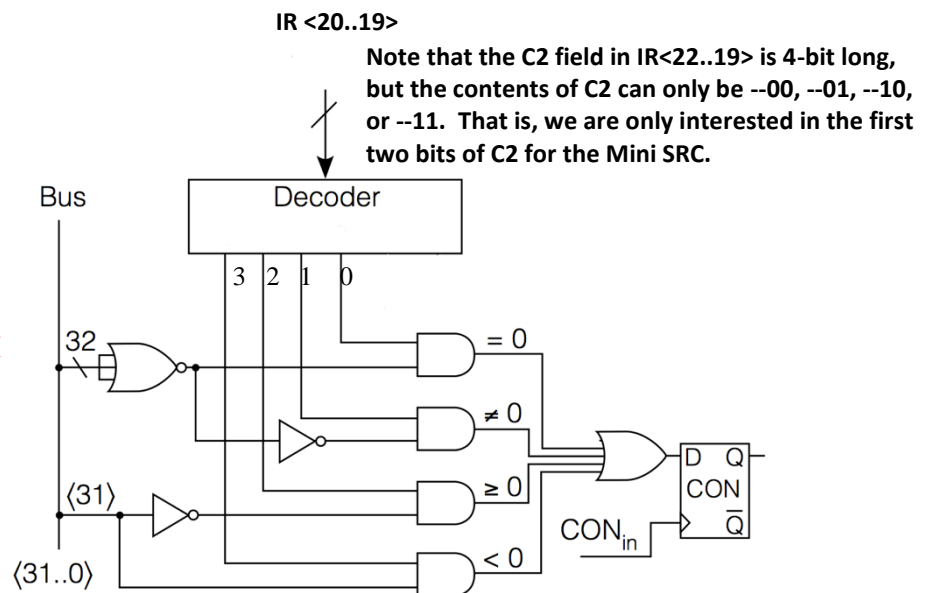


Figure 7. Computation of the conditional value CON in the CON FF Logic

2.5 Input, Output ports

The Input and Output Ports are shown in Figure 8. The input device may generate a strobe signal to indicate when the data is available. Depending on your design, you may (or may not) need the *Strobe* or the *Clock* signal.

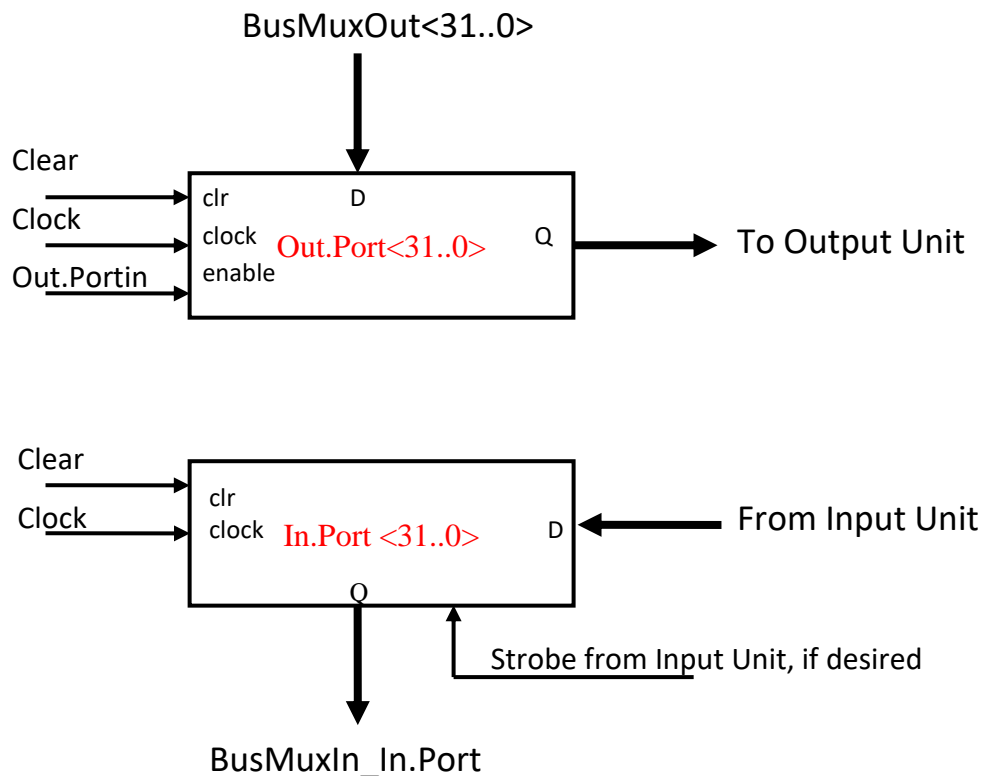


Figure 8. Input and Output ports

3. Lab Procedure

Add the necessary logic discussed in Section 2, in that order, to your Datapath in Phase 1. Then, using the following control sequences, test your logic circuits for the *ld*, *ldi*, *st*, *addi*, *andi*, *ori*, *brzr*, *brnz*, *brmi*, *brpl*, *jr*, *jal*, *mfhi*, *mflo*, *out*, and *in* instructions. Again, **you are advised to functionally simulate your design as you go through the different design steps.**

3.1 Load Instructions – *ld* and *ldi*:

In order to test your RAM and the memory interface logic, functionally simulate the *ld* and *ldi* instructions by using the following Control Sequences (depending on your memory subsystem, you may need to come up with similar Control Sequences). As in Phase 1, cycles T0, T1, and T2 are used for the instruction fetch. The selection of a register or the value 0 is affected by the BAout control signal. Sign extension is accomplished by the Cout control signal.

Mdatain[31..0] has been provided in T1 and T6 for clarity and should not be regarded as input signal in your simulations anymore. Instead, the memory data should now come directly from your RAM memory output data.

Control Sequence: *ld*

<u>Step</u>	<u>Control Sequence</u>
T0	PCout, MARin, IncPC, Zin
T1	Zlowout, PCin, Read, Mdatain[31..0], MDRin
T2	MDRout, IRin
T3	Grb, BAout, Yin
T4	Cout, ADD, Zin
T5	Zlowout, MARin
T6	Read, Mdatain[31..0], MDRin
T7	MDRout, Gra, Rin

Control Sequence: *ldi*

<u>Step</u>	<u>Control Sequence</u>
T0-T2	Same as before for "Instruction Fetch"
T3	Grb, BAout, Yin
T4	Cout, ADD, Zin
T5	Zlowout, Gra, Rin

Demonstrate to the TA the proper operation of your memory interface logic and RAM by simulating the following instructions. You will need to preload your registers and the contents of the RAM with some known values. You may initialize the memory in Verilog or VHDL in different ways. In Verilog, for example, you may use [\\$readmemh](#) function to initialize the memory with a text file with hexadecimal values, separated by whitespace. In Quartus, you may create a **Memory Initialization File (.mif)** as an input file under File > New > Memory Files > Memory Initialization File. Consult [Intel document here](#).

Case 1:	<i>ld</i>	R2, 0x95
Case 2:	<i>ld</i>	R0, 0x38(R2)
Case 3:	<i>ldi</i>	R2, 0x95
Case 4:	<i>ldi</i>	R0, 0x38(R2)

3.2 Store Instruction - *st*:

In order to test your RAM and the memory interface logic, functionally simulate the *st* instruction for the following cases. Devise your own Control Sequence, inferred from the control sequence for the *ld* instruction. In your simulations, show that the memory location with the address 0x87 for Case 1, and (R1) + 0x87 for Case 2 is loaded with the value 0x43 in R1, respectively. Thus, for verification purposes, you may need to read back the contents of these memory locations. Demonstrate your simulations to one of the TAs in the Lab.

Case 1:	<i>st</i>	0x87, R1
Case 2:	<i>st</i>	0x87(R1), R1

3.3 ALU Immediate Instructions – addi, andi, ori:

Demonstrate the functionality of your “Add immediate” instruction by simulating the Control Sequence for *addi R3, R4, -5* instruction, as follows:

Control Sequence: addi

<u>Step</u>	<u>Control Sequence</u>
T0-T2	Same as before for “Instruction Fetch”
T3	Grb, Rout, Yin
T4	Cout, ADD, Zin
T5	Zlowout, Gra, Rin

Demonstrate the operation of your “AND immediate” and “OR immediate” instructions by simulating the Control Sequence for *andi R3, R4, 0x53* and *ori R3, R4, 0x53* instructions, respectively. The Control Sequences are the same as the one for *addi* instruction except for using the AND/OR control signal in T4 instead of the ADD signal.

3.4 Branch instructions – brzr, brnz, brpl, brmi:

In order to test the “CON FF” logic, functionally simulate the *brzr*, *brnz*, *brpl*, and *brmi* instructions by using the following Control Sequence.

Control Sequence: Branch

<u>Step</u>	<u>Control Sequence</u>
T0-T2	Same as before for “Instruction Fetch”
T3	Gra, Rout, CONin
T4	PCout, Yin
T5	Cout, ADD, Zin
T6	Zlowout, CON → PCin

// IF CON FF = 1, THEN
PCin ← PC + 1 + C (sign-extended)
// See if there is any way of doing this better

Verify your implementation by simulating the following Conditional Branch instructions:

Case 1:	brzr	R5, 14
Case 2:	brnz	R5, 14
Case 3:	brpl	R5, 14
Case 4:	brmi	R5, 14

Preload the register R5 and the PC, so the branch will be “taken” or “not taken”. Demonstrate your simulation to one of the TAs in the Lab.

3.5 Jump Instructions – jr, jal:

Demonstrate the functionality of *jr* instruction by simulating the Control Sequence for *jr R6* instruction. Preload the register involved.

Control Sequence: jr

<u>Step</u>	<u>Control Sequence</u>
T0-T2	Same as before for “Instruction Fetch”
T3	Gra, Rout, PCin

Derive the control sequence for *jal* instruction and demonstrate its functionality by simulating the Control Sequence for *jal R6* instruction. Preload the register involved.

3.6 Special Instructions - mfhi and mflo:

Derive the control sequences for *mfhi* and *mflo* instructions and demonstrate their functionality to one of the TAs by simulating the Control Sequences for *mfhi R6* and *mflo R7* instructions. Preload the registers involved.

3.7 Input/output Instructions – in, out:

Demonstrate the functionality of your Output Port logic by simulating the control sequence for *out R3* instruction. Preload the register involved.

Control Sequence: out

<u>Step</u>	<u>Control Sequence</u>
T0-T2	Same as before for “Instruction Fetch”
T3	Gra, Rout, Out.Port

In order to test your Input Port logic, functionally simulate the *in R4* instruction. Demonstrate your simulations to one of the TAs in the Lab.

4. Report:

Upload your Phase 2 report (one per group) in PDF format to onQ by 11:59pm on the day of your Phase 2 demo. Phase 2 report consists of:

- Your Verilog/VHDL code (and schematic, if any)
- Your testbenches (if they are similar, include one testbench and discuss the differences for the other cases).
- Printout of the contents of memory
- Functional simulation runs for all the instructions in Phase 2 (Sections 3.1 to 3.7)